

# Digital-electronics-1


## Labs/05-counter

Dominik Grenčík, 220815

Digital-electronics-1
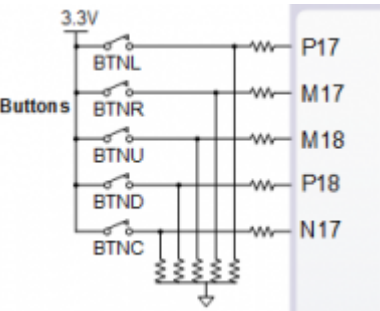
### 1. Preparation tasks

- Figure and table with connection of push buttons on Nexys A7 board



Buttons	Board
BTNL	P17
BTNR	M17
BTNU	M18
BTND	P18
BTNC	N17

- Table with calculated values

Time interval	Number of clk periods	Number of clk periods in hex	Number of clk periods in binary
2 ms	200 000	x"3_0d40"	b"0011_0000_1101_0100_0000"
4 ms	400 000	x"6_1a80"	b"0110_0001_1010_1000_0000"
10 ms	1 000 000	x"f_4240"	b"1111_0100_0010_0100_0000"
250 ms	25 000 000	x"17d_7840"	b"0001_0111_1101_0111_1000_0100_0000"
500 ms	50 000 000	x"2fa_f080"	b"0010_1111_1010_1111_0000_1000_0000"
1 sec	100 000 000	x"5f5_e100"	b"0101_1111_0101_1110_0001_0000_0000"

### 2. Bidirectional counter

- Listing of VHDL code of the process p\_cnt\_up\_down

```
p_cnt_up_down : process(clk)
begin
    if rising_edge(clk) then

        if (reset = '1') then          -- Synchronous reset
            s_cnt_local <= (others => '0'); -- Clear all bits

        elsif (en_i = '1') then        -- Test if counter is enabled

            -- TEST COUNTER DIRECTION HERE
            if (cnt_up_i = '1') then
                s_cnt_local <= s_cnt_local + 1;
            elsif (cnt_up_i = '0') then
                s_cnt_local <= s_cnt_local - 1;
            end if;
        end if;
    end if;
end process p_cnt_up_down;
```

- Listing of VHDL reset and stimulus processes from testbench file tb\_cnt\_up\_down.vhd

```
-----
-- Reset generation process
-----
p_reset_gen : process
begin
    s_reset <= '0';
    wait for 12 ns;

    -- Reset activated
    s_reset <= '1';
    wait for 73 ns;

    s_reset <= '0';
    wait;
end process p_reset_gen;

-----
-- Data generation process
-----
p_stimulus : process
begin
    report "Stimulus process started" severity note;

    -- Enable counting
    s_en      <= '1';

    -- Change counter direction
```

```


s_cnt_up <= '1';
wait for 230 ns;
s_cnt_up <= '0';
wait for 180 ns;

-- Disable counting
s_en      <= '0';

report "Stimulus process finished" severity note;
wait;
end process p_stimulus;

```

 - Screenshot with simulated time waveforms



### 3. Top level

- Listing of VHDL code from source file top.vhd

```

-----
-- Architecture body for top level
-----

architecture Behavioral of top is

    -- Internal clock enable
    signal s_en : std_logic;
    -- Internal counter
    signal s_cnt : std_logic_vector(4 - 1 downto 0);

begin

    -----
    -- Instance (copy) of clock_enable entity
    clk_en0 : entity work.clock_enable
        generic map(
            --- WRITE YOUR CODE HERE
            g_MAX => 1000000000
        )
        port map(
            --- WRITE YOUR CODE HERE
            clk  => CLK100MHZ,
            reset => BTNC,
            ce_o  => s_en
        );

```

```

-----
-- Instance (copy) of cnt_up_down entity
bin_cnt0 : entity work.cnt_up_down
  generic map(
    --- WRITE YOUR CODE HERE
    g_CNT_WIDTH => 4
  )
  port map(
    --- WRITE YOUR CODE HERE
    clk          => CLK100MHZ,
    reset        => BTNC,
    en_i         => s_en,
    cnt_up_i     => SW(0),
    cnt_o        => s_cnt
  );

```

```

-- Display input value on LEDs
LED(3 downto 0) <= s_cnt;

```

```

-----
-- Instance (copy) of hex_7seg entity
hex2seg : entity work.hex_7seg
  port map(
    hex_i    => s_cnt,
    seg_o(6) => CA,
    seg_o(5) => CB,
    seg_o(4) => CC,
    seg_o(3) => CD,
    seg_o(2) => CE,
    seg_o(1) => CF,
    seg_o(0) => CG
  );

```

```

-- Connect one common anode to 3.3V
AN <= b"1111_1110";

```

```

end architecture Behavioral;

```

- Image of the top layer

