

# Digital-electronics-1

---

## Labs/02-logic

Dominik Grenčík, 220815

[Digital-electronics-1](#)

---

### 1. Binary comparator truth table

Dec. equivalent	B[1:0]	A[1:0]	B is greater than A	B equals A	B is less than A
0	0 0	0 0	0	1	0
1	0 0	0 1	0	0	1
2	0 0	1 0	0	0	1
3	0 0	1 1	0	0	1
4	0 1	0 0	1	0	0
5	0 1	0 1	0	1	0
6	0 1	1 0	0	0	1
7	0 1	1 1	0	0	1
8	1 0	0 0	1	0	0
9	1 0	0 1	1	0	0
10	1 0	1 0	0	1	0
11	1 0	1 1	0	0	1
12	1 1	0 0	1	0	0
13	1 1	0 1	1	0	0
14	1 1	1 0	1	0	0
15	1 1	1 1	0	1	0

$$\begin{aligned}
 equals_{SOP}^{canon} &= (\overline{B_1} \cdot \overline{B_0} \cdot \overline{A_1} \cdot \overline{A_0}) + (\overline{B_1} \cdot B_0 \cdot \overline{A_1} \cdot A_0) + (B_1 \cdot \overline{B_0} \cdot A_1 \cdot \overline{A_0}) + (B_1 \cdot B_0 \cdot A_1 \cdot A_0) \\
 less_{POS}^{canon} &= (B_1 + B_0 + A_1 + A_0) \cdot (B_1 + \overline{B_0} + A_1 + A_0) \cdot (B_1 + \overline{B_0} + A_1 + \overline{A_0}) \cdot (\overline{B_1} + B_0 + A_1 + A_0) \cdot (\overline{B_1} + B_0 + A_1 + \overline{A_0}) \cdot \\
 &= (\overline{B_1} + B_0 + \overline{A_1} + A_0) \cdot (\overline{B_1} + \overline{B_0} + A_1 + A_0) \cdot (\overline{B_1} + \overline{B_0} + A_1 + \overline{A_0}) \cdot (\overline{B_1} + \overline{B_0} + \overline{A_1} + A_0) \cdot (\overline{B_1} + \overline{B_0} + \overline{A_1} + \overline{A_0})
 \end{aligned}$$


---

### 2. 2-bit comparator

#### Karnaughove mapy

- Equals SoP

		A1 A0			
		00	01	11	10
B1 B0	00	1			
	01		1		
	11			1	
	10				1

- Greater SoP

		A1 A0			
		00	01	11	10
B1 B0	00				
	01	1			
	11	1	1		1
	10	1	1		

- Less PoS

		A1 A0			
		00	01	11	10
B1 B0	00	0			
	01	0	0		
	11	0	0	0	0
	10	0	0		0

$$greater_{SoP}^{min} = (B_1 \cdot \overline{A_1}) + (B_1 \cdot B_0 \cdot \overline{A_0}) + (B_0 \cdot \overline{A_1} \cdot \overline{A_0})$$

$$less_{PoS}^{min} = (\overline{B_1} + A_1) \cdot (\overline{B_0} + A_1) \cdot (A_1 + A_0) \cdot (\overline{B_1} + \overline{B_0}) \cdot (\overline{B_1} + A_0)$$

[EDA Playgrounds 2-bit comparator](#)

### 3. 4-bit comparator

- **Listing of VHDL architecture from design file (design.vhd)**

```

-----
--
-- Example of 4-bit binary comparator using the when/else assignment.
-- EDA Playground
--
-- Copyright (c) 2020-2021 Tomas Fryza
-- Dept. of Radio Electronics, Brno University of Technology, Czechia
-- This work is licensed under the terms of the MIT license.
--
-----

library ieee;
use ieee.std_logic_1164.all;

```

```

-----
-- Entity declaration for 2-bit binary comparator
-----
entity comparator_4bit is
    port(
        a_i          : in  std_logic_vector(4 - 1 downto 0);
        b_i          : in  std_logic_vector(4 - 1 downto 0);

        -- COMPLETE ENTITY DECLARATION
        B_greater_A_o : out std_logic;
        B_equals_A_o  : out std_logic;
        B_less_A_o    : out std_logic      -- B is less than A
    );
end entity comparator_4bit;

-----
-- Architecture body for 2-bit binary comparator
-----
architecture Behavioral of comparator_4bit is
begin
    B_greater_A_o <= '1' when (b_i > a_i) else '0';
    B_equals_A_o  <= '1' when (b_i = a_i) else '0';
    B_less_A_o    <= '1' when (b_i < a_i) else '0';

    -- WRITE "GREATER" AND "EQUALS" ASSIGNMENTS HERE

end architecture Behavioral;

```

- **Listing of VHDL stimulus process from testbench file (testbench.vhd)**

```

-----
--
-- Testbench for 4-bit binary comparator.
-- EDA Playground
--
-- Copyright (c) 2020-2021 Tomas Fryza
-- Dept. of Radio Electronics, Brno University of Technology, Czechia
-- This work is licensed under the terms of the MIT license.
--
-----

library ieee;
use ieee.std_logic_1164.all;

-----
-- Entity declaration for testbench
-----
entity tb_comparator_4bit is

```

```

-- Entity of testbench is always empty
end entity tb_comparator_4bit;

-----
-- Architecture body for testbench
-----

architecture testbench of tb_comparator_4bit is

    -- Local signals
    signal s_a      : std_logic_vector(4 - 1 downto 0);
    signal s_b      : std_logic_vector(4 - 1 downto 0);
    signal s_B_greater_A : std_logic;
    signal s_B_equals_A  : std_logic;
    signal s_B_less_A    : std_logic;

begin
    -- Connecting testbench signals with comparator_4bit entity (Unit Under Test)
    uut_comparator_4bit : entity work.comparator_4bit
        port map(
            a_i      => s_a,
            b_i      => s_b,
            B_greater_A_o => s_B_greater_A,
            B_equals_A_o  => s_B_equals_A,
            B_less_A_o    => s_B_less_A
        );

    -----
    -- Data generation process
    -----

    p_stimulus : process
    begin
        -- Report a note at the beginning of stimulus process
        report "Stimulus process started" severity note;

        -- First test values
        s_b <= "0000"; s_a <= "0000"; wait for 100 ns;
        -- Expected output
        assert ((s_B_greater_A = '0') and (s_B_equals_A = '1') and (s_B_less_A =
'0'))
        -- If false, then report an error
        report "Test failed for input combination: 0000, 0000" severity error;

        -- First test values
        s_b <= "0000"; s_a <= "0001"; wait for 100 ns;
        -- Expected output
        assert ((s_B_greater_A = '0') and (s_B_equals_A = '0') and (s_B_less_A =
'1'))
        -- If false, then report an error
        report "Test failed for input combination: 0000, 0001" severity error;

        -- First test values
        s_b <= "0100"; s_a <= "0010"; wait for 100 ns;
        -- Expected output

```

```

    assert ((s_B_greater_A = '1') and (s_B_equals_A = '0') and (s_B_less_A =
'0'))
    -- If false, then report an error
    report "Test failed for input combination: 0100, 0010" severity error;

    -- First test values
    s_b <= "0101"; s_a <= "0110"; wait for 100 ns;
    -- Expected output
    assert ((s_B_greater_A = '0') and (s_B_equals_A = '0') and (s_B_less_A =
'1'))
    -- If false, then report an error
    report "Test failed for input combination: 0101, 0110" severity error;

    -- First test values
    s_b <= "0110"; s_a <= "0110"; wait for 100 ns;
    -- Expected output
    assert ((s_B_greater_A = '0') and (s_B_equals_A = '1') and (s_B_less_A =
'0'))
    -- If false, then report an error
    report "Test failed for input combination: 0110, 0110" severity error;

    -- First test values
    s_b <= "0110"; s_a <= "0111"; wait for 100 ns;
    -- Expected output
    assert ((s_B_greater_A = '0') and (s_B_equals_A = '0') and (s_B_less_A =
'1'))
    -- If false, then report an error
    report "Test failed for input combination: 0110, 0111" severity error;

    -- First test values
    s_b <= "0111"; s_a <= "0010"; wait for 100 ns;
    -- Expected output
    assert ((s_B_greater_A = '1') and (s_B_equals_A = '0') and (s_B_less_A =
'0'))
    -- If false, then report an error
    report "Test failed for input combination: 0111, 0010" severity error;

    -- First test values
    s_b <= "0111"; s_a <= "0111"; wait for 100 ns;
    -- Expected output
    assert ((s_B_greater_A = '0') and (s_B_equals_A = '1') and (s_B_less_A =
'0'))
    -- If false, then report an error
    report "Test failed for input combination: 0111, 0111" severity error;

    -- First test values
    s_b <= "1000"; s_a <= "0011"; wait for 100 ns;
    -- Expected output
    assert ((s_B_greater_A = '1') and (s_B_equals_A = '0') and (s_B_less_A =
'0'))
    -- If false, then report an error
    report "Test failed for input combination: 1000, 0011" severity error;

    -- First test values

```

```

s_b <= "1011"; s_a <= "1101"; wait for 100 ns;
-- Expected output
assert ((s_B_greater_A = '0') and (s_B_equals_A = '0') and (s_B_less_A =
'1'))
-- If false, then report an error
report "Test failed for input combination: 1011, 1101" severity error;

-- First test values
s_b <= "1110"; s_a <= "1000"; wait for 100 ns;
-- Expected output
assert ((s_B_greater_A = '0') and (s_B_equals_A = '0') and (s_B_less_A =
'1'))
-- If false, then report an error
report "Test failed for input combination: 1110, 1000" severity error;

-- Report a note at the end of stimulus process
report "Stimulus process finished" severity note;
wait;
end process p_stimulus;

end architecture testbench;

```

- **Listing of simulator console output, i.e. with one reported error**

```

[2021-02-20 13:21:53 EST] ghdl -i design.vhd testbench.vhd && ghdl -m
tb_comparator_4bit && ghdl -r tb_comparator_4bit --vcd=dump.vcd && sed -i
's/^U/X/g; s/^-/X/g; s/^H/1/g; s/^L/0/g' dump.vcd
analyze design.vhd
analyze testbench.vhd
elaborate tb_comparator_4bit
testbench.vhd:51:9:@0ms:(report note): Stimulus process started
testbench.vhd:127:9:@1100ns:(assertion error): Test failed for input combination:
1110, 1000
testbench.vhd:133:9:@1100ns:(report note): Stimulus process finished
Finding VCD file...
./dump.vcd
[2021-02-20 13:21:54 EST] Opening EPWave...
Done

```

[EDA Playgrounds 4-bit comparator](#)